

EE313 Laboratory #1

Diode Characterization and Differential Temperature Sensor

- A. Design a method to measure I_s of a p-n diode.
- B. Design a differential temperature sensor using the temperature dependence of a diode forward voltage under constant current with the following specifications (all in the room temperature between 18°C to 28°C.)
 - 1. When the sensor is at room temperature, the output voltage should be nearly half the supply voltage ($V_{dd}/2 \pm 0.3V$).
 - 2. The output voltage should show the temperature difference between the room temperature and the temperature of the sensor diode in degrees with a 10% tolerance. For example, a +1-degree difference should give us a change of $+1 \pm 0.1$ V in the output voltage.
 - 3. A red LED should turn on when the sensor's temperature exceeds $+3 \pm 0.5^\circ\text{C}$ the room temperature.
 - 4. The LED should never flicker around the thresholds (it should have a 0.1°C hysteresis).

You are allowed to use only one supply voltage of less than 15 V. Try to minimize the number of components used.

Preliminary work (Due Feb. 11, 2024)

- A. Simulate your method to determine I_s of the diode. Compare the finding with the spice model value of I_s .
- B. Simulate your design using LTSpice to show that all specifications are satisfied. You may need one adjustable trimmer resistor to achieve accurate temperature-to-voltage mapping.

The default temperature of simulation in LTSpice is 27°C. This can be changed, for example, to 22°C by adding the spice directive

`.temp 22`

LTSPICE allows setting the device temperature of a component. However, this possibility is not described in the documentation. Control right-click on the diode body and add "`temp={t1}`" to one of the empty attribute fields after the diode model name (for example, Value2). Then add

`.step param t1 begin end stepsize`

Spice directive to see the response as a set of curves with different temperatures.

Provide a schematic of your design, showing a component list. Use Diptrace to generate the schematic. Refer to the Diptrace Tutorial.

Experimental work (Due Feb. 18, 2024)

- A. Apply your method to measure I_s of a 1N4148 diode.
- B. Build your temperature sensor design on a breadboard. You may use a resistor in physical contact with the sensor diode and insulate it with electrical tape to adjust the sensor temperature. The resistor may be connected to a separate adjustable voltage source to heat the sensor in a controlled manner. Connect your multimeter to the output. Show that it satisfies all the specifications. It is always a good idea to place a decoupling capacitor (100nF) between the

supply voltage and the ground. You may use a thermocouple provided with many multimeters to measure the room and sensor temperatures and calibrate the resistive heater.

Grading criteria:

Preliminary work (10 pts)

I_s measurement method with LTSpice simulation: 3pts

Nice looking temperature sensor schematic with component list: 1pt

Minimized component count of the temperature sensor design: 2pts

Satisfaction of all four criteria in LTSpice: 4pts, 1 pt each

Experimental work (10 pts)

I_s measurement: 3pts

A neat, easy-to-follow, and easy-to-debug circuit implementation on the breadboard. 1pt

Experimental satisfaction of all four criteria: 6 pts, 1.5pt each

Preliminary work (10 pts)

Minimized number of components: 3pt

Nice looking schematic with component list: 1pt

Satisfaction of all four criteria in LTSpice: 6pts, 1.5 pts each

Experimental work (10 pts)

A neat, easy-to-follow, and easy-to-debug circuit implementation on the protoboard. 2pts

Experimental satisfaction of all four criteria: 8 pts, 2pts each