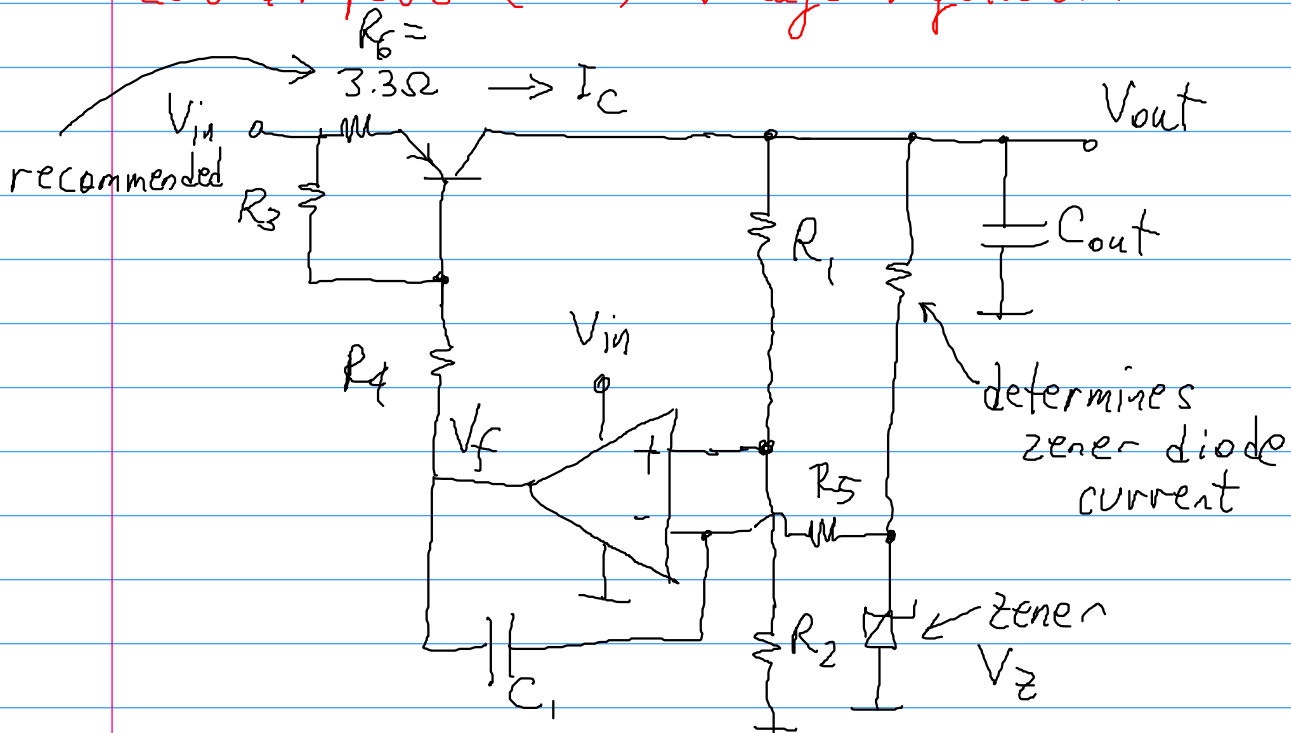


Low-Dropout (LDO) voltage regulator:



$$V_{out} \frac{R_2}{R_1 + R_2} = V_Z \Rightarrow V_{out} = V_Z \frac{R_1 + R_2}{R_2}$$

C_1 needed for stability. $f = \frac{1}{2\pi R_5 C_1}$ ← Freq. Band of feedback

When $V_f = 0 \Rightarrow$ Maximum I_C

Regulation is present if OPAMP is not saturated.

OPAMP is not sat, if $0 < V_f < V_{in} - 2$

β , R_6 , R_3 , R_4 , and V_{in} determines the short circuit current.